

Equation & Units: [units in square brackets]

$$V=IR \quad [1 \text{ V}=1 \text{ A}\cdot\Omega]$$

$$P=IV \quad [1 \text{ W}=1 \text{ A}\cdot\text{V}]$$

$$R_s=R_1+R_2+\dots$$

$$\frac{1}{R_p}=\frac{1}{R_1}+\frac{1}{R_2}+\dots$$

$$1/C_s=1/C_1+1/C_2+1/C_3+\dots$$

$$C_p=C_1+C_2+C_3+\dots$$

$$V_C=Q/C \quad [1 \text{ V}=1 \text{ C/F}]$$

$$\tau_{RC}=RC \quad [1 \text{ s}=1 \Omega\cdot\text{F}]$$

$$V_L=L(di/dt) \quad [1 \text{ V}=1 \text{ H}\cdot\text{A/s}]$$

$$\tau_{RL}=L/R \quad [1 \text{ s}=1 \text{ H}/\Omega]$$

$$|X_C|=1/\omega C=1/2\pi fC$$

$$Z_C=-j/\omega C=-j/2\pi fC \quad [\Omega=1/\text{Hz}\cdot\text{F}] \quad j=\sqrt{-1}$$

$$|X_L|=\omega L=2\pi fL$$

$$Z_L=j\omega L=j2\pi fL \quad [\Omega=\text{Hz}\cdot\text{H}] \quad \omega=2\pi f$$

$$V=\sqrt{(V_{\text{real}})^2+(V_{\text{imaginary}})^2}$$


$$\phi=\tan^{-1}(V_{\text{imaginary}}/V_{\text{real}})$$

$$\tilde{V}=Ve^{j\phi_v}$$

$$\tilde{A}\times\tilde{B}=A\times Be^{j(\phi_A+\phi_B)}$$

$$\tilde{A}/\tilde{B}=(A/B)e^{j(\phi_A-\phi_B)}$$

$$\tilde{v}=\tilde{i}\tilde{Z}$$

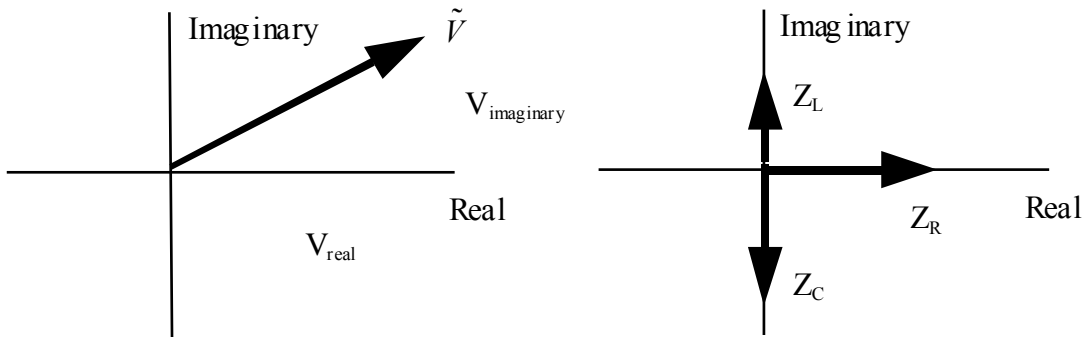

$$\frac{v_s}{v_p}=\frac{N_s}{N_p}$$

$$P_p\approx P_s$$

$$\frac{Z_s}{Z_p}=\left(\frac{N_s}{N_p}\right)^2$$

$$C\approx\frac{i}{\Delta V\cdot f} \quad [F=A/(V\cdot\text{Hz})]$$

$$r=\frac{\Delta V}{V_{DC}}$$

$$V_p=\sqrt{2}\cdot V_{rms}$$

$$I_B=I_E-I_C$$

$$I_C=\beta I_B$$

$$V_E=V_B-0.6 \text{ V}$$

$$V_{out}=A(V_+-V_-)$$

Golden Rules for Ideal Op Amps with negative feedback:

1. The output will adjust in any way possible to make the inverting input and the non-inverting input terminals equal in voltage.
2. The inputs draw no current.

Nyquist criterion: $f_{\text{sample}} > 2f_{\text{max}}$

$$\frac{\text{Integer}}{2^n}=\frac{V_{\text{analog}}}{V_{\text{max}}}$$