



# Mid-Term Prep

## Chapter 1-5 Equations

$$\Delta V = -IR$$

$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} + \dots$$

$$R_s = R_1 + R_2 + \dots$$

$$P = IV$$

$$\Delta v_C = -Q/C$$

$$C_p = C_1 + C_2 + \dots$$


$$\frac{1}{C_s} = \frac{1}{C_1} + \frac{1}{C_2} + \dots$$

$$dv_C/dt = -i/C$$

$$\mathbf{t}_{RC} = RC$$

$$j = \sqrt{-1}$$

$$\Delta \tilde{v} = -i \tilde{Z}$$

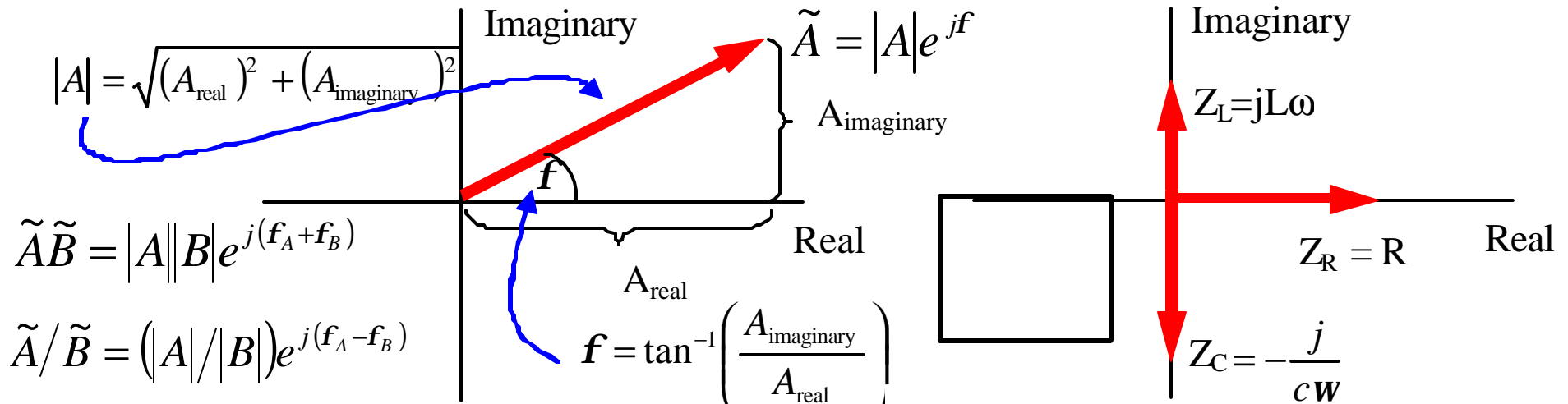

$$\Delta V \approx \frac{i}{C \cdot f}$$

$$r = \frac{\Delta V}{V_{DC}}$$

$$V_p = \sqrt{2} \cdot V_{rms}$$

$$\frac{Z_s}{Z_p} = \left(\frac{N_s}{N_p}\right)^2$$

$$P_p \approx P_s \quad \frac{v_s}{v_p} = \frac{N_s}{N_p}$$

$$I_B = I_E - I_C$$

$$I_C = \mathbf{b}I_B$$

$$V_E = V_B - 0.6 \text{ V}$$

# Mid-Term Prep


## Chapter 1

$$\Delta V = -IR \quad [1 \text{ V} = 1 \text{ A} \cdot \Omega]$$

$$P = IV \quad [1 \text{ W} = 1 \text{ A} \cdot \text{V}]$$

$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} + \dots$$

$$R_s = R_1 + R_2 + \dots$$

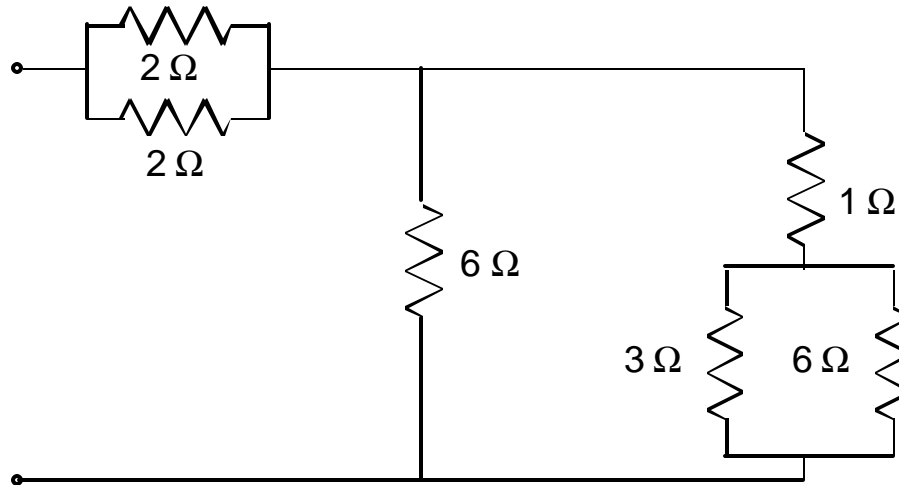

- Reduce the combination of resistors shown in the circuit above to a single equivalent resistor.
- Calculate the current through the 3- $\Omega$  resistor and the voltage across the 1- $\Omega$  resistor when a 120-V source is attached across the terminals.

# Mid-Term Prep


## Chapter 1

$$\Delta V = -IR \quad [1 \text{ V} = 1 \text{ A} \cdot \Omega]$$

$$P = IV \quad [1 \text{ W} = 1 \text{ A} \cdot \text{V}]$$

$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} + \dots$$

$$R_s = R_1 + R_2 + \dots$$

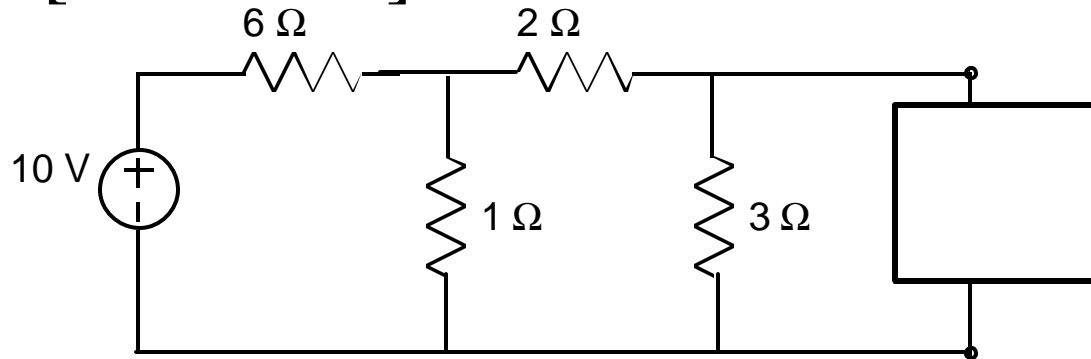

- Replace the network to the left of the slot by its Thévenin equivalent circuit.
- If a 10-Ω resistor is inserted in the slot, calculate the current through it.

# Mid-Term Prep


## Chapter 2

$$\Delta v_C = -Q/C \quad [1 \text{ V} = 1 \text{ C/F}]$$

$$dv_C/dt = -i/C \quad \mathbf{t}_{RC} = RC \quad [1 \text{ s} = 1 \text{ } \Omega \cdot \text{F}]$$

$$C_p = C_1 + C_2 + C_3 + \dots$$
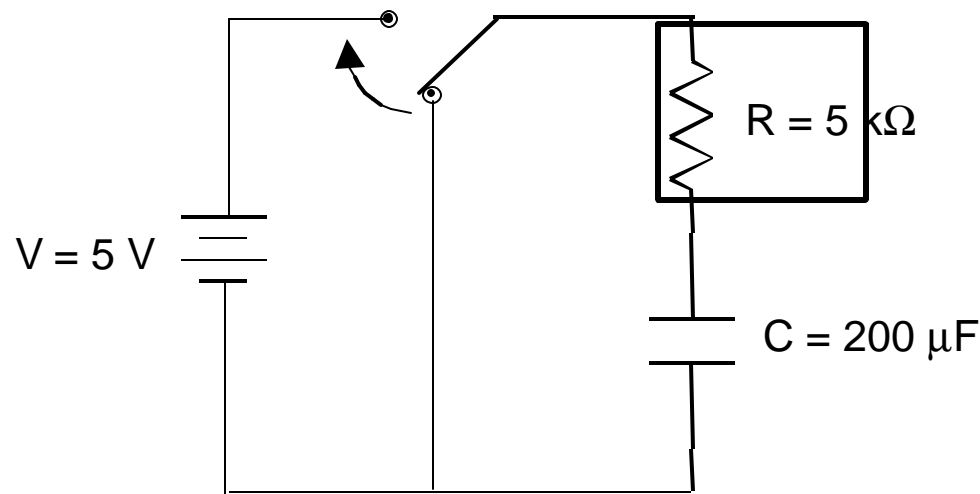
$$1/C_s = 1/C_1 + 1/C_2 + 1/C_3 + \dots$$



- Determine the initial current through the resistor just after the switch is flipped.
- Determine the voltage across the capacitor 3 s after the switch is flipped.

# Mid-Term Prep


## Chapter 3

$$j = \sqrt{-1}$$

$$\tilde{A}\tilde{B} = |A||B|e^{j(f_A+f_B)}$$

$$\Delta\tilde{v} = -\tilde{i}\tilde{Z}$$

$$\tilde{A}/\tilde{B} = (|A|/|B|)e^{j(f_A-f_B)}$$

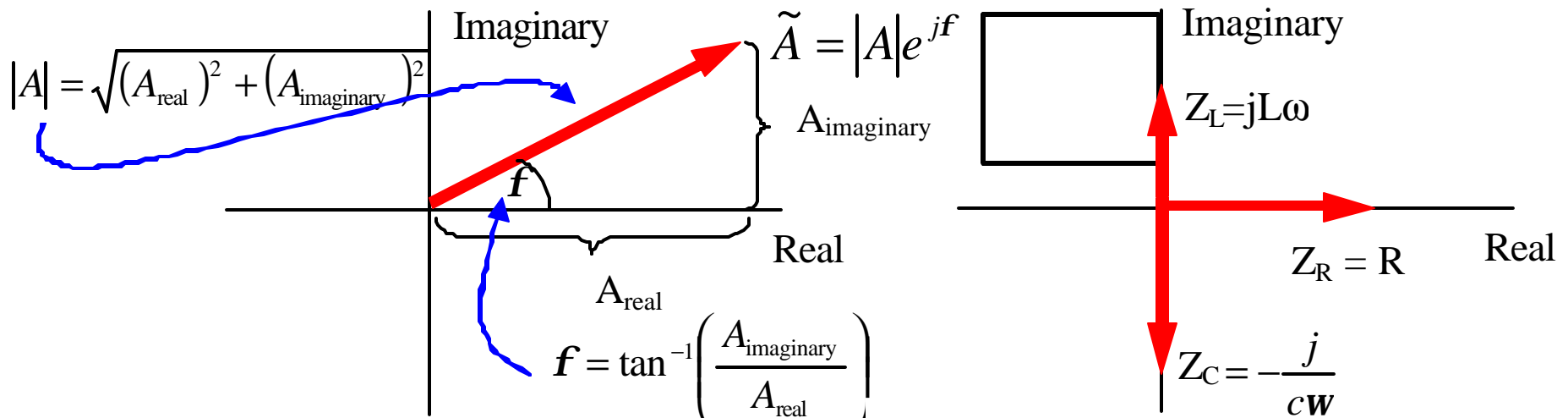

A 4- $\Omega$  resistor in series with a 7.96-mH inductor is connected to a 110-V 60-Hz source.

- Determine the impedance of the circuit.
- Determine the current flowing in the circuit.


# Mid-Term Prep

## Chapter 4

$$\Delta V \approx \frac{i}{C \cdot f}$$

$$r = \frac{\Delta V}{V_{DC}}$$

$$V_p = \sqrt{2} \cdot V_{rms}$$

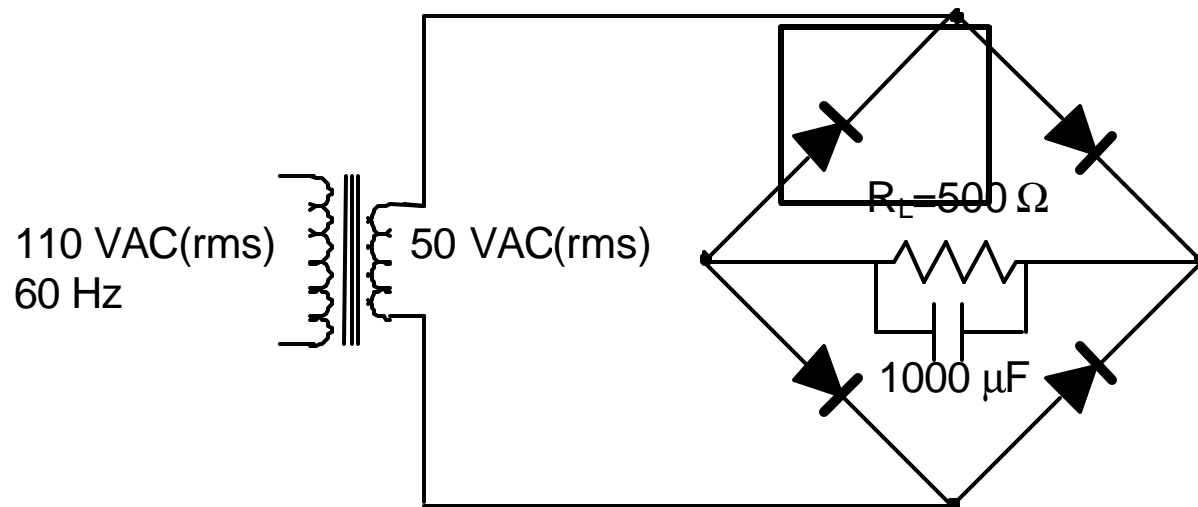

For the rectifier circuit above:

- What would the peak voltage across and current through the resistor be without the capacitor? (You should take into account the voltage drops across the diodes.)
- With the capacitor in place how much does the voltage across the resistor vary? (You may assume that the current remains very close to its maximum value.)
- What is the ripple factor for the circuit?


# Mid-Term Prep

## Chapter 4

$$\frac{v_s}{v_p} = \frac{N_s}{N_p}$$

$$P_p \approx P_s$$
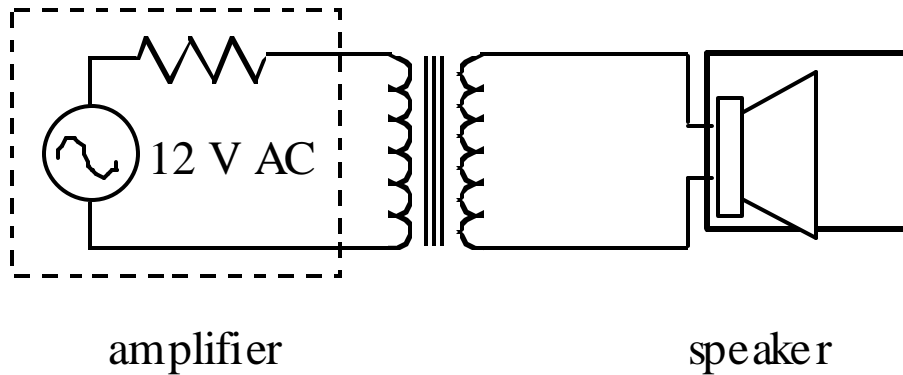
$$\frac{Z_s}{Z_p} = \left( \frac{N_s}{N_p} \right)^2$$



An amplifier with an output resistance of  $50 \text{ k}\Omega$  is going to be used to drive an  $8\text{-}\Omega$  speaker. Determine the turns ratio for a transformer that will provide maximum power transfer to the speaker.  
What is the power delivered to the speaker?




# Mid-Term Prep

## Chapter 5

$$I_B = I_E - I_C$$

$$I_C = \beta I_B$$

$$V_E = V_B - 0.6 \text{ V}$$

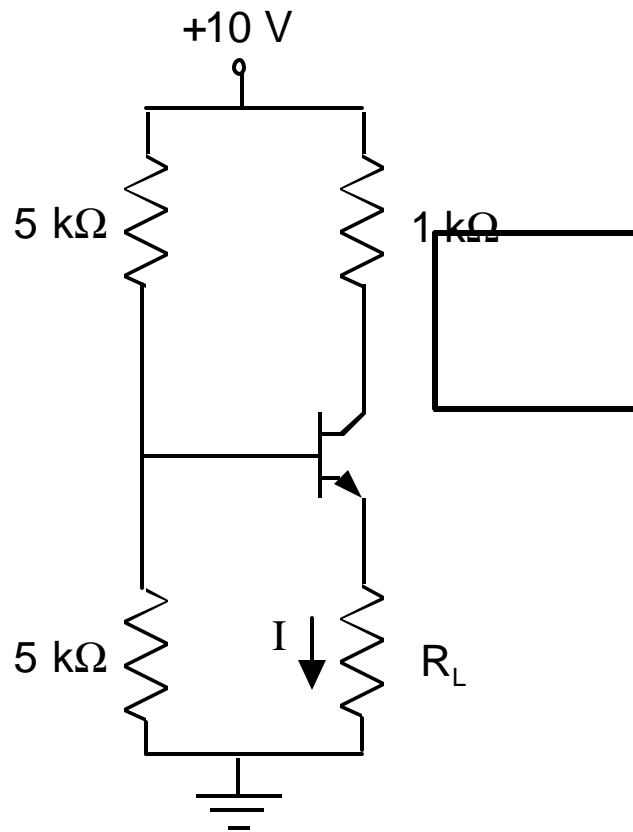

What is the current ( $I$ ) through the load resistor as a function of  $R_L$ ?

