

Physics 310
Lecture 10 – Microprocessors

Mon. 3/29 Wed. 3/31 Thurs. 4/1 Fri. 4/2	Project: Component Shopping Ch 13: Microprocessor Basics Intro to Projects More Ch 13	Project Progress Report (due at the beginning of class)
Mon. 4/5 Wed. 4/7 Thurs. 4/8 Fri. 4/9	Projects Projects Projects Projects	
Mon. 4/12 Wed. 4/14 Thurs. 4/15 Fri. 4/16	Projects Projects Projects Review	Project Report & Notebook
Mon. 4/19	Demonstrate Projects	
Final Exam: Thursday April 22nd 3:00 p.m. or Saturday April 24th 9:00 a.m. / 12:00 noon (we'll choose as a class)		

Announcements:

- **Parts have been ordered; they should be in later this week.**
- **Most of you didn't actually 'turn in' your project progress reports. Please do so (I'll make photo copies and return them).**

13.1 Intro:

The microprocessor is the natural conclusion of our study of digital circuitry. This is where all the 'thinking' or processing happens inside a computer or other common electronic devices. At the time that the text was written, microprocessors were finding their way into our daily lives, off the desktop and into our cars, ovens, etc. Today, they've found their way into our constant companions – phones and mp3 players.

13.2 Computer Arithmetic


The book mentions Hexadecimal representation and bits (one data line) bytes (eight data lines) and nibbles (four data lines) as well as KB (2^{10}) and MB (2^{20}). For our purposes though, it's probably not worth focusing much on these.

Computers were originally for *computing* / *calculating*, and they still do a lot of this. So a natural bridge from logic gates to computers (and microprocessors) is considering how these gates can be used to perform common computational tasks: addition, subtraction, and multiplication.

Binary Addition

You may recall that I'd introduced the simple "half adder" just after we'd met binary (to suggest that studying binary wasn't such a non-sequeter after studying logic gates). Now I'll use the text's notation

Physics 310
Lecture 10 – Microprocessors

 


Inputs		Outputs			
Augend	Addend	Sum	Carry		
A	B	C 2 ⁰	C 2 ¹		
0	+	0	=	0	0
0	+	1	=	1	0
1	+	0	=	1	0
1	+	1	=	0	1

Alone, this is of fairly limited use – it can at most add two one-bit numbers and thus add one plus one to get two. Before we consider how we'd use gates to add *two*-bit binary numbers, let's first consider how we add 'two-bit' decimal numbers. It's probably been a long time since you've actually thought through the words you were taught in your early days of addition:

1 6	“six plus five	1	1 6	“two plus one	1	1 6	“three plus	1
+2 5	->	1 6	->	+2 5	->	3 1	+2 5	->
		1		1		3 1	4 1	

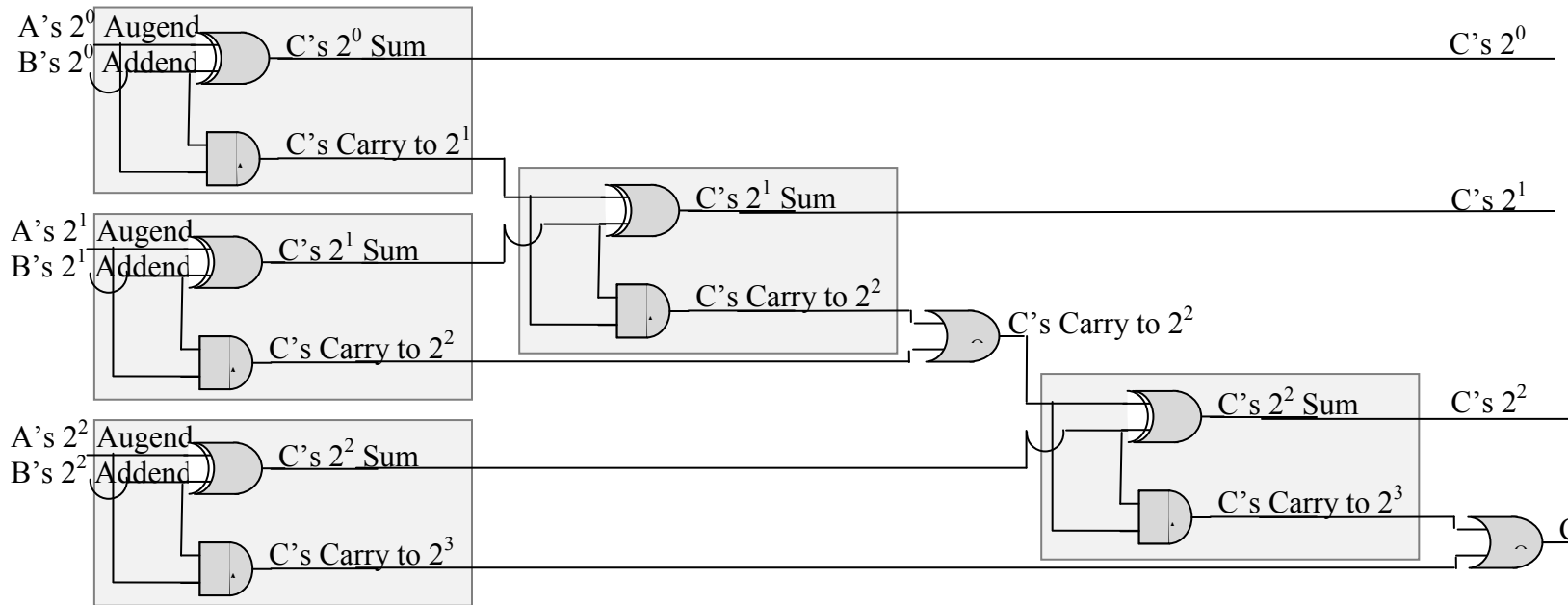We essentially do the same thing when adding a two-bit binary number: we first add the lowest bits 2^0 , in the process we generate the answer's lowest bit, and the “carry” which we carry over to add to the sum of the next lowest bit, and so on until we don't have any more bits to add.



So, we add the 2^0 bits and carry to the 2^1 ; we add the 2^1 bits and then add the carry in and

Physics 310
Lecture 10 – Microprocessors

determine the carry out, then we add the 2^2 bit, add the carry in and determine the carry out,...

As for determining the “carry out,” the OR gate is because two additions determine the answer’s 2^1 place value and *either* one of those (but not both) can be responsible for generating a carry to the 2^2 addition. The same thing happens when we add familiar decimal numbers. Consider these two examples, again, spelled out as if we were in third grade,

		1		1 1	1 1
1 6 9		1 6 9		1 6 9	1 6 9
<u>+2 5 3</u> ->		<u>+2 5 3</u> ->		<u>+2 5 3</u>	<u>+2 5 3</u> ...
		2		1 2	1 2
					2 2

Note: the carry to the 100’s place is generated now

Alternatively, if we’d added $149 + 253$, then we wouldn’t be carrying to the 100’s place until we added in the carry from the 1’s place. So, the carry to the next place can happen during either addition operation, but not during both (you only ever “carry the one” never “carry the two”.)

In figure 13.4B, the book shows the inner workings of a 4-bit adder. The exact logic used is a little different from that illustrated here, but it gets the job done. With the help of some of the binary logic identities in chapter 11, one may be able to translate between the two; alternatively, the logic tables can be generated and compared.


Binary Subtraction

First think about how you do subtraction with multi-‘bit’ decimal numbers.

Borrow 1 from 3 to make 14	Borrow 1 from 7 to make 12
7 3 4	7 2 (14)
<u>-6 4 8</u>	<u>-6 4 8</u>
	6
	6 (12) (14)
	<u>-6 4 8</u> ...
	6

So, we need a ‘borrowing’ mechanism for our subtraction. That has to essentially accomplish four things: a) subtract the value from the 2^{n+1} bit of the Minuend, b) add it to the next 2^n bit of the Minuend, c) only do this if the 2^n bit of the Minuend is less than that of the Subtrahend, and d) actually subtract the bits.

Here’s the circuitry that accomplishes these tasks for one bit.

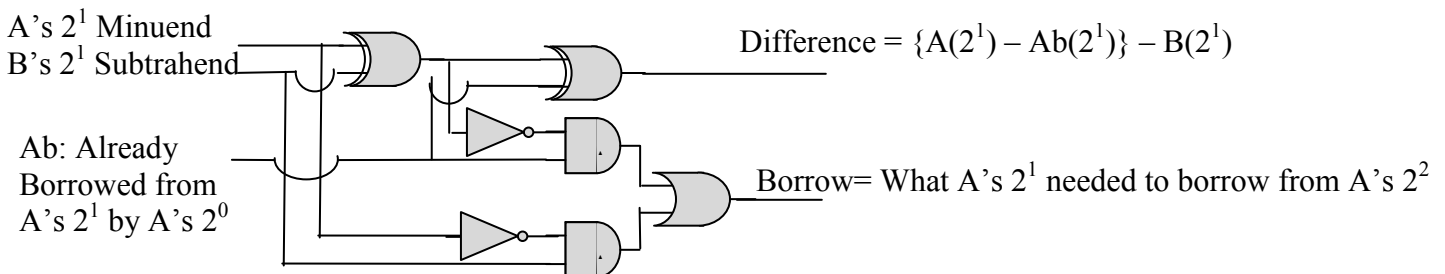

Physics 310
Lecture 10 – Microprocessors

Note: what the book confusingly labeled Bin, I've labeled Ab: what the previous bit of A already borrowed from this one. Let's see if we can reason out the truth table:

Minuend A's 2^1	Subtrahend B's 2^1	Borrowed <i>from</i> A's 2^1 by A's 2^0	Difference	Borrowed <i>by</i> A's 2^1 from A's 2^2
0	0	0	0	0
0	1	0	1	1
1	0	0	1	0
1	1	0	0	0
0	0	1	1	1
0	1	1	0	1
1	0	1	0	0
1	1	1	1	1

Two's-Complement Arithmetic

From the perspective of minimizing the amount of hardware necessary, it would be nice to be able to handle subtraction with the *exact same circuitry* as we use for addition. Of course, subtracting a positive number is the same as adding a negative number, so the real question is, how can we represent a *negative* number in binary *such that* when we use our adding circuitry we get the appropriate result.

How do we need to represent a negative number?

1. First off, we give up the Most Significant Bit as denoting a number, instead it tells us the *sign* of the number, in that way we can represent both positive and negative numbers. The price we pay is that we have smaller range of numbers that we can represent. Okay, that sounds reasonable enough. Now, given that,
2. We “complement” all the bits – replace 1's with 0's and vice versa (easily done with inverters on the bit's lines.)
3. We add 1 to the last bit (easily done with our addition circuitry.)

First, let's perform this operation a few times, and then see that the resulting representation of a negative number adds to give the right answer.

Represent -63:

$$\begin{array}{r}
 63 = 0011\ 1111 \\
 \overline{63} = 1100\ 0000 \\
 \quad \quad \quad +1 \\
 \hline
 -63 = 1100\ 0001
 \end{array}$$

Represent -28:

$$\begin{array}{r}
 28 = 0001\ 1100 \\
 \overline{28} = 1110\ 0011 \\
 \quad \quad \quad +1 \\
 \hline
 -28 = 1110\ 0100
 \end{array}$$

Now, let's add a negative number to a positive one:

$$\begin{array}{r}
 63 = 0011\ 1111 \\
 +(-28) = 1110\ 0100 \\
 \hline
 35 = (1) 0010\ 0011
 \end{array}$$

(we just ditch the extra 'carried' 1)

